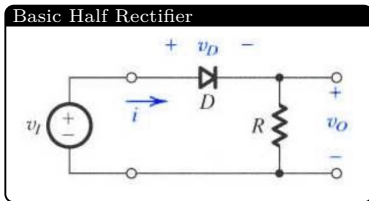


DC Diode Analysis

Either know voltages and treat as open/short circuits, or guess and check.




Ideal Diode Rectifier Conduction Angle

$$2\theta = 2\cos^{-1}\left(\frac{V_S^{\text{fwd}}}{V_S^{\text{amp}}}\right)$$

Selecting Peak Inverse Voltage
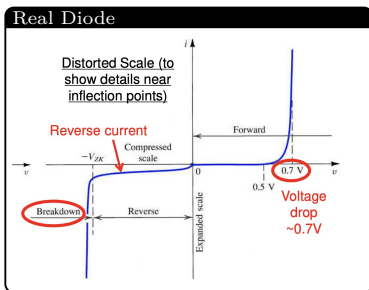
$$\text{PIV}_{\text{des}} = 1.5\text{PIV}$$



Real Diode Model

$$i = I_S \left(\exp\left(\frac{v}{nV_T}\right) - 1 \right)$$


$$V_T = \frac{kT}{q}$$

$n = 1, k = 1.38 \cdot 10^{-23} \text{ J/K}, q = 1.602 \cdot 10^{-19} \text{ C}, T = 300\text{K}.$

Simplified Diode Model

For $i \gg I_S$ or $v > 10nV_T$:

$$i \approx I_S e^{v/nV_T}$$

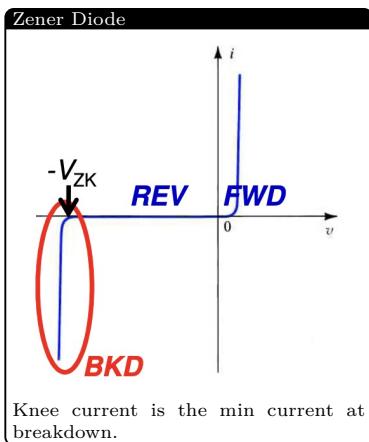

Iterative Analysis for Diodes

$$V_{DD} = IR + V \quad (1)$$


$$I = I_S (e^{V/V_T} - 1) \quad (2)$$

$$I_S \approx xe^{-0.7/V_T} \quad (3)$$

- Using your guess for V , calculate I from (1).
- Substitute I into (2) to get a new value for V .
- Substitute V back into (1) to get a value for I .

Continue iterating until:

$$\frac{(I_n - I_{n-1})}{I_n} \leq 1\%$$

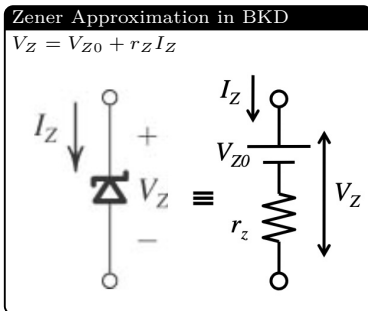

Zener Regulators

$$V_0 = V_{Z0} \frac{\frac{R}{R_L}}{r_Z + \frac{R}{R_L}} + V^+ \frac{\frac{r_Z}{R_L}}{R + \frac{r_Z}{R_L}}$$

$$\Delta V_0 = \Delta V^+ \frac{\frac{R}{R_L}}{R + \frac{R}{R_L}}$$


$$V_0 = V_{Z0} + \frac{V^+ - V_0}{R} r_Z$$

Line Regulation

$$\left. \frac{\Delta V_0}{\Delta V^+} \right|_{I_L=\text{constant}} = \frac{r_Z}{R + r_Z}$$

Load Regulation

$$\left. \frac{\Delta V_0}{\Delta I_L} \right|_{V^+=\text{constant}} = -\frac{r_Z}{R}$$

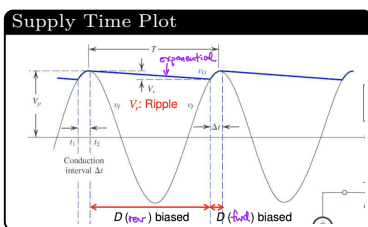

Ripple Voltage – Full Rectifier

$$V_r \approx \frac{V_p T}{2R_L C} = \frac{V_p}{2fR_L C}$$

Ripple Voltage – Half Rectifier

$$V_r \approx \frac{V_p T}{R_L C} = \frac{V_p}{fR_L C}$$

Input Voltage

$$V_p \approx V_o = V_p - \frac{1}{2}V_r \approx V_p$$

$$\approx V_p \left(\frac{4fR_L C - 1}{4fR_L C} \right)$$

Load Current

$$I_L \approx \frac{R_L}{V_L} = \frac{V_p - \frac{1}{2}V_r}{R_L} \approx \frac{V_p}{R_L}$$

Half Rectifier Average Output Voltage

$$V_o^{\text{avg}} = V_p - V_D - \frac{1}{2}V_r$$

Conduction Angle

$$\omega \Delta t = \sqrt{\frac{2V_r}{V_p}}$$

Max Diode Current

$$i_D^{\text{max}} \approx I_L \left(1 + 2\pi \sqrt{\frac{2V_p}{V_r}} \right)$$

Average Diode Current

$$i_D^{\text{ave}} \approx I_L \left(1 + \pi \sqrt{\frac{2V_p}{V_r}} \right)$$

Peak Inverse Voltage 2-Diode


$$\text{PIV} = 2V_p$$

Peak Inverse Voltage 4-Diode

$$\text{PIV} = V_p$$

Average Voltage

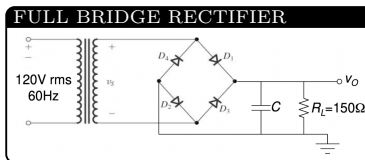You just have to integrate and divide by the total period (2π).



Peak Voltage for Bridge Supply

$$V_{\text{max}} = V_p - 2V_d$$

Conduction Time Fraction

$$\tau = \frac{\pi - 2\theta}{2\pi}$$

Substitutions for Real Case Constant Voltage Drop

Half-Wave

$$V_p \rightarrow V_p - V_D$$

$$\text{PIV} = 2V_p - V_D$$

$$= (V_p - V_D) - (-V_p)$$




Full-Wave

$$V_p \rightarrow V_p - V_D \quad (2D)$$

$$V_p \rightarrow V_p - 2V_D \quad (4D)$$

$$\text{PIV} \approx 2V_p - V_D \quad (2D)$$
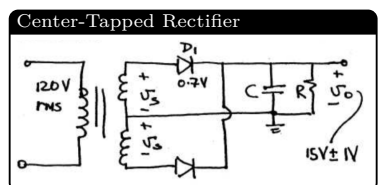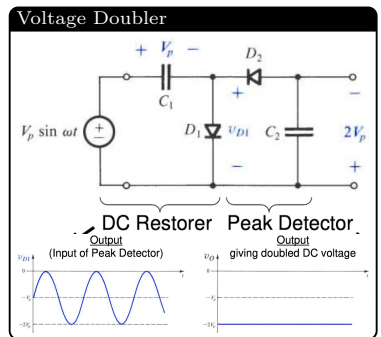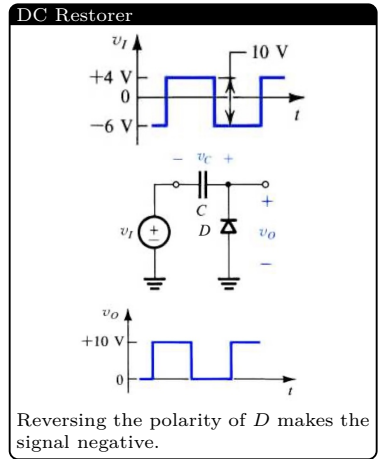
$$\text{PIV} \approx V_p - V_D \quad (4D)$$





Required Output Voltage for Supply

$$V_{\text{req}} = V_{o, \text{des}} + V_D + \Delta V_{o, \text{des}}$$

Required Secondary RMS

$$V_p = \frac{nV_{\text{req}}}{\sqrt{2}}$$

n is the number of equispaced "taps".

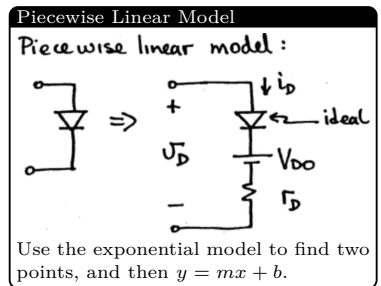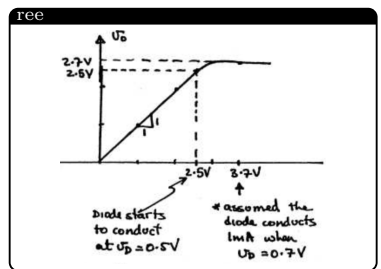

Clipping Circuit

$$v_o = \begin{cases} L_+ & v_i > \frac{L_+}{K} \\ K v_i & \frac{L_-}{K} \leq v_i \leq \frac{L_+}{K} \\ L_- & v_i < \frac{L_-}{K} \end{cases}$$

Intrinsic Carrier Concentration for Pure Silicon

$$n_i^2 = BT^3 \exp\left(-\frac{E_g}{kT}\right)$$

where:

$E_g = 1.12\text{eV}$: band gap

T : temperature

$k = 8.62 \times 10^{-5}\text{eV/K}$: Boltzmann constant

$B = 5.4 \times 10^{31}$

Fraction of Ionized Atoms

$$\frac{n_i}{N}$$

Conductivity

$$\sigma = q(p\mu_p + n\mu_n)$$

Where:

p : Concentration of free holes

n : Concentration of free electrons

μ_p : Mobility of holes

(RT: $480\text{cm}^2/\text{V}\cdot\text{s}$)

μ_n : Mobility of electrons

(RT: $1350\text{cm}^2/\text{V}\cdot\text{s}$)

$q = 1.6 \times 10^{-19}\text{C}$: Electron charge

Charge Neutrality Relationship

$$N_D + p = N_A + n$$

N_D : Concentration of donor atoms

N_A : Concentration of acceptor atoms

Resistance

$$R = \frac{\rho L}{A}$$

where $\rho = \frac{1}{\sigma}$ (resistivity).

Law of Mass Action

$$n_i^2 = pn$$

Note: n_i for silicon is generally

$1.45 \times 10^{10}\text{cm}^{-3}$.

Diffusion Current for Holes

$$J_{p,\text{diffn}} = -qD_p \frac{dp}{dx}$$

Where $D_p = 34\text{cm}^2/\text{s}$ at 300K

Diffusion Current for Electrons

$$J_{n,\text{diffn}} = -qD_n \frac{dn}{dx}$$

Where $D_p = 12\text{cm}^2/\text{s}$ at 300K

Total Diffusion Current Density

$$J_{\text{diffn}} = J_{p,\text{diffn}} + J_{n,\text{diffn}}$$

Drift Current Density

$$J = \sigma E$$

Drift Current

$$I = \sigma E \cdot A$$

Mobility-Diffusivity Relationship (Einstein)

$$\frac{D_n}{\mu_n} = \frac{D_p}{\mu_p} = V_T$$

Where V_T is thermal voltage.

Drift Velocity

$$v_{\text{drift},p/n} = \mu_{p/n} E$$

Thermal Voltage

$$V_T = \frac{kT}{q}$$

$k = 1.38 \times 10^{-23}$

$q = 1.6 \times 10^{-19}$

Built-In Voltage

$$V_0 = V_T \ln\left(\frac{N_A N_D}{n_i^2}\right)$$

Depletion Region Width

$$W_{\text{dep}} = \sqrt{\frac{2\epsilon_s}{q} \left(\frac{1}{N_A} + \frac{1}{N_D}\right) (V_0 - V)}$$

$\epsilon_s = 1.04 \times 10^{-12}\text{F/cm}$ (Dielectric constant of Si)


Charge in a Junction

$$qJ = qNV$$

Drift Current pt2

$$J_{\text{drift}} = qp\mu_p E + qn\mu_n E$$

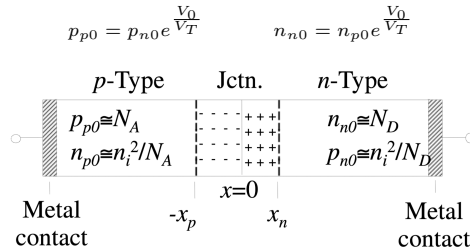Concentration Relationships: Open Circuit




Common Mode Rejection Ratio

$$\text{CMRR} = 20 \log\left(\frac{|A_d|}{|A_{cm}|}\right)$$


Op-Amp Golden Rules

1. Infinite Open Loop Gain ($A \rightarrow \infty$)
2. No current flow through the inputs
3. Potential difference between input pins is zero


Weighted Summer

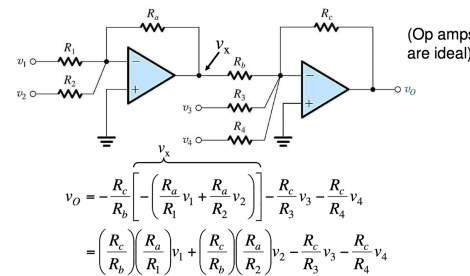

Inverting Amplifier

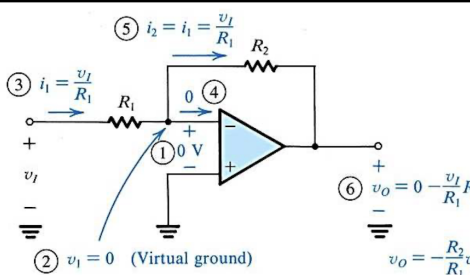

Non-Inverting Amplifier

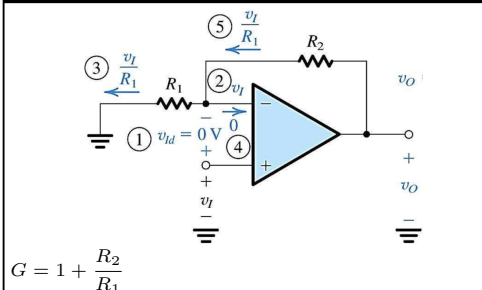

Charge Density at Depletion Region

$$\rho_p = -qN_A \quad \rho_n = qN_D$$

Charge Balancing

$$qN_A x_p A = qN_D x_n A \quad \text{or} \quad \frac{x_n}{x_p} = \frac{N_A}{N_D}$$

Depletion Zone Boundaries

$$x_p = W_{\text{dep}} \frac{N_D}{N_A + N_D} \quad x_n = W_{\text{dep}} - x_p$$

Electric Field at Center of Depletion Zone


$$E(0) = -\frac{qN_A}{\epsilon_s} x_p$$

Differential Amplifier – Common Mode Gain


$$A_{cm} = \frac{v_o}{v_{Icm}} = \left(\frac{R_4}{R_4 + R_3} \right) \left(1 - \frac{R_2 R_3}{R_1 R_4} \right)$$

If ideal, can assume an error for $\frac{R_2 R_3}{R_1 R_4} = \gamma$ to calculate CMRR.


Ideal Differential Amplifier

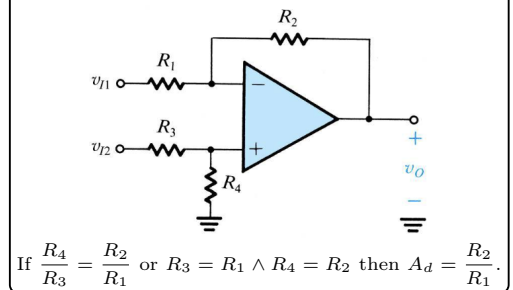


Bistable Multivibrator

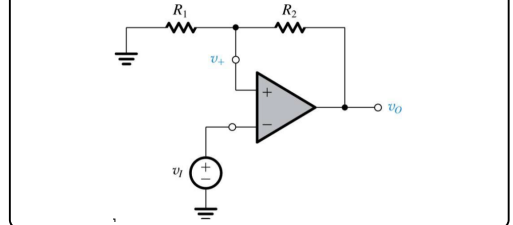

Hysteresis in Multivibrator Circuit

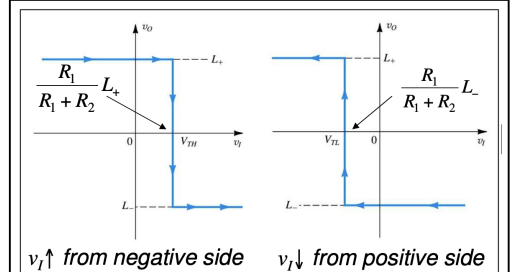

Monostable Multivibrator

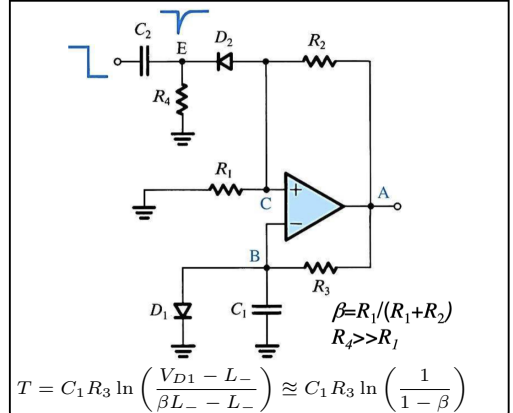

Monostable Multivibrator – Min Trigger Voltage

$$v_{t,\text{min}} = \beta L_+ - V_{D2} + V_{D1}$$

Monostable Multivibrator – Recovery Time

$v_B = L_- - (L_- - V_{D1})e^{-t/(C_1 R_3)}$

Setting $v_B = V_{\text{diode}}$, one can solve for the recovery time.

Non-Ideal Inverting Opamp Gain

$$G = \frac{-\frac{R_f}{R_{in}}}{1 + \frac{R_f}{A}}$$